

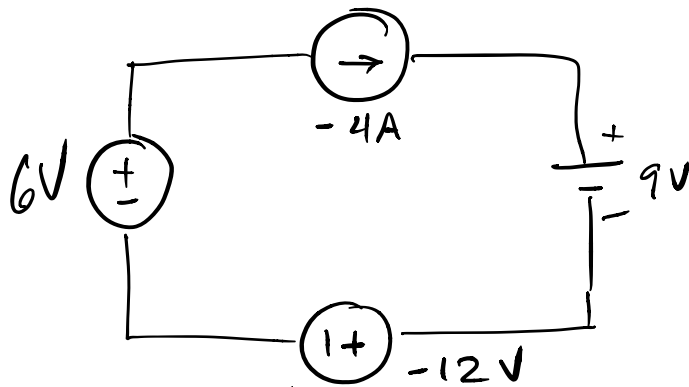


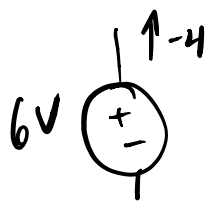

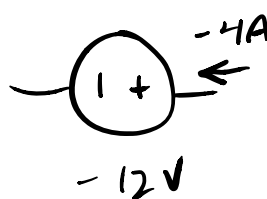
$$P_{6V} = \overset{\text{rise}}{-} V I = -6 \cdot -4 = 24W \quad (\text{dissipating})$$



$$P_{-12V} = + V I = -12 \cdot -4 = 48W \quad (\text{diss.})$$


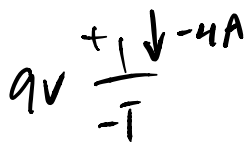
$$P_{9V} = + V I = +9 \cdot -4 = -36W \quad (\text{or } 36W \text{ gen.})$$



by Conservation of Power :

watch signs!!!


$$\sum P = P_{6V} + P_{-12V} + P_{9V} + P_{-4A} = 0$$

$$P_{-4A} = -P_{6V} - P_{-12V} - P_{9V} = -24 - 48 - 36$$

$P_{-4A} = -36W$ or 36W generating

KVL :


CW, LLH

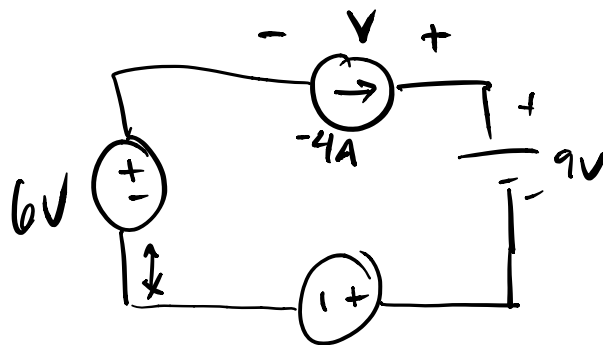

$$\begin{aligned}
 & \begin{array}{c} \text{rise} \\ \downarrow \end{array} -6 \quad \begin{array}{c} \text{drop} \\ \downarrow \end{array} V \quad \begin{array}{c} \text{drop} \\ \downarrow \end{array} 9 \quad \begin{array}{c} \text{drop} \\ \downarrow \end{array} (-12) = 0 \\
 & V = -6 + 9 - 12 = \boxed{-9V}
 \end{aligned}$$

$$\begin{aligned}
 P_{4A} &= -V \cdot I = -(-9) \cdot -4 \\
 &= \underline{\underline{-36W}} \quad \checkmark
 \end{aligned}$$

Resistors

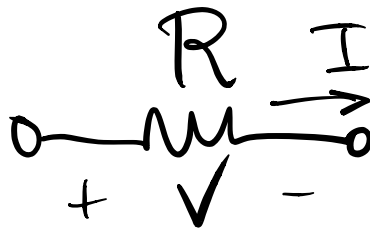

- .. two-terminal device that opposes the flow of current
- .. unit : ohm (Ω)

Ohm's Law :

$$R = \frac{V}{I} \text{ or } V = IR \text{ or } I = \frac{V}{R}$$

.. resistors can only dissipate power!

Passive device

∞ voltage always drops in the direction of positive current!!!

power in a resistor :

$$P = VI$$

$$\infty P = I \cdot R \cdot I = \underbrace{I^2 R}$$

$$\text{OR } P = V \cdot \frac{V}{R} = \underbrace{\frac{V^2}{R}}$$


.. physical resistors have a resistance and power rating.

.. small resistors used in electronics :


$\frac{1}{8}W, \frac{1}{4}W, \frac{1}{2}W, 1W, 2W, \uparrow$

- .. small carbon film resistors in kb: $\frac{1}{4}W$, 5% tolerance
- .. significance of power rating is that resistors dissipate power by giving off heat.
 - .. power rating is just as important as value!
 - .. for long life and reliability, derate
(use higher power rating than necessary)

factor of three
→ good idea!

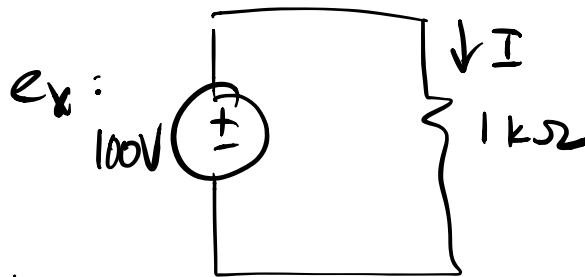

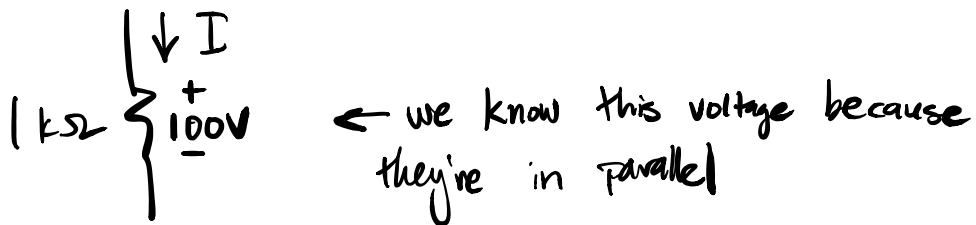- .. determine I and power dissipated in resistor




$$I = \frac{V}{R} = \frac{100V}{1k} = \underline{\underline{100mA}}$$


- .. if circuit is entirely in kΩ and V, currents will be in mA → save steps, but be careful!

G	giga	10^9	$P = \frac{V^2}{R}$ $= \frac{100^2}{1k}$ $= 10,000 \text{ mW}$
M	mega	10^6	
k	kilo	10^3	
m	milli	10^{-3}	
μ	micro	10^{-6}	
n	nano	10^{-9}	OR <u>10 W</u>
p	pico	10^{-12}	
f	femto	10^{-15}	

ex:-

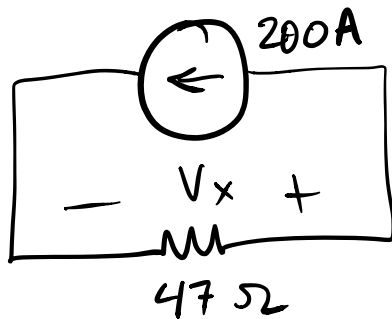

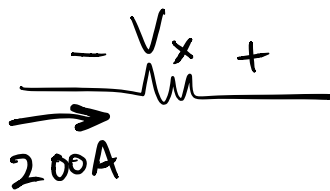.. determine V_x
and the power in
the resistor



rise!

$$-V_x = IR$$

$$V_x = -IR$$

$$= -200 \cdot 47$$


$$V_x = -9400 \text{ V}$$

or -9.4 kV

$$P = I^2 R = 200^2 \cdot 47 = 1.88 \text{ MW}$$

Resistors in Series

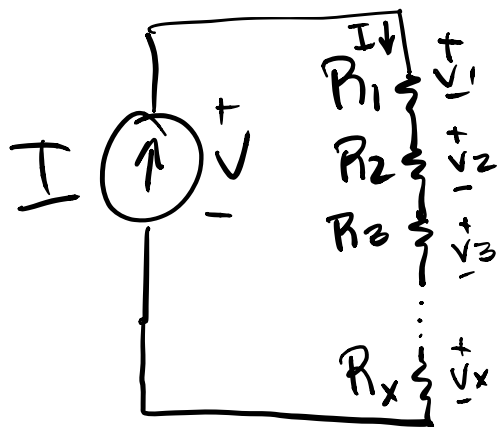.. consider a number of resistors in series, connected to a current source



.. We know by Ohm's Law :

$$V_1 = I R_1$$

$$V_2 = I R_2$$

etc..

.. We know by KVL :

$$-V + V_1 + V_2 + \dots + V_x = 0$$

$$V = I R_1 + I R_2 + \dots + I R_x$$

.. the equivalent resistance "seen" by the current source is

$$R = \frac{V}{I} = \frac{\cancel{I} R_1 + \cancel{I} R_2 + \dots + \cancel{I} R_n}{\cancel{I}}$$

$$R_{\text{series}} = R_1 + R_2 + \dots + R_n$$

.. Resistors in series add

.. if all equal-value resistors:

$$R_{\text{series}} = nR$$

.. the reciprocal of resistance is conductance

Homework:
read S: M
2.4 - 2.8

G

Unit: siemens
or ohm^{-1}

or mho ($\sim$)

↙ upside-down
omega !!

$$G = \frac{1}{R}$$

$$G_{\text{series}} = \frac{1}{\frac{1}{G_1} + \frac{1}{G_2} + \dots + \frac{1}{G_n}}$$