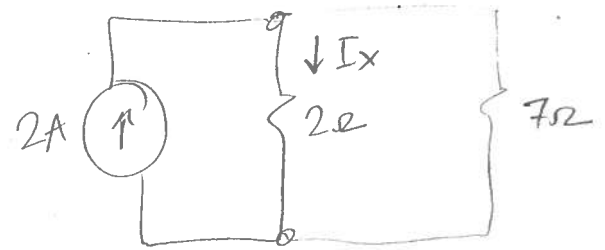
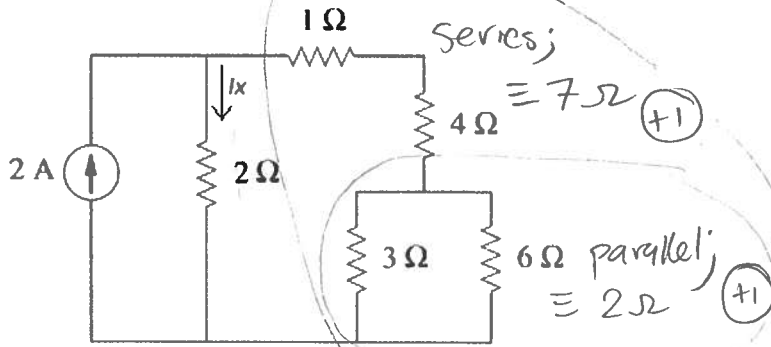



1) Use current division to determine I_x .

$$R_{eq} = 2\Omega \parallel 7\Omega = \frac{14}{9}\Omega \quad (+1)$$

$$\therefore I_x = 2 \left(\frac{14/9}{2} \right) \quad (+1)$$

$$I_x = 14/9 \text{ A} \quad (+1)$$

or 1.556 A

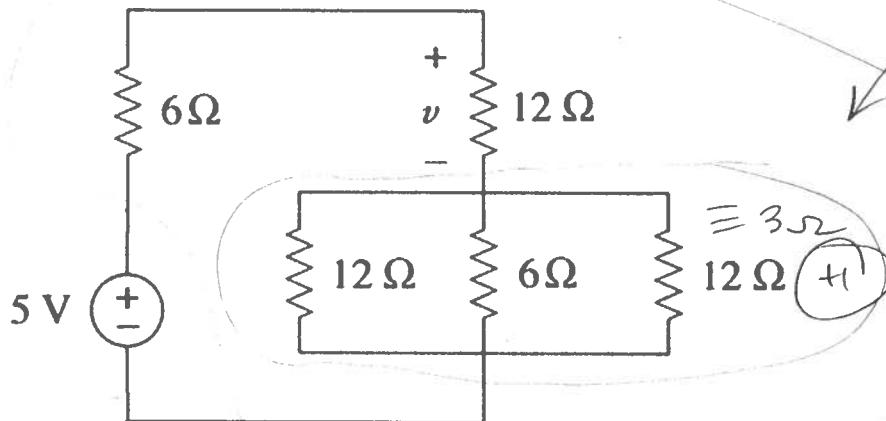2) Use voltage division to find v .

$$R_{eq} = 6\Omega + 12\Omega + 3\Omega = 21\Omega \quad (+1)$$

$$\therefore v = 5 \left(\frac{12}{21} \right) = \frac{20}{7} \text{ V} \quad (+1)$$


or 2.85 V

11

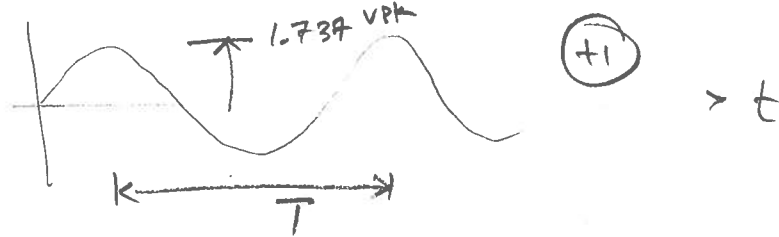4) Sketch a $1.228 V_{RMS}$ sine wave with a frequency of 1 kHz , indicating the peak amplitude and period. Also sketch the current waveform that would result if this voltage was applied to a $600\text{-}\Omega$ resistor. Determine the power in the resistor.

$$V_{pk} = V_{RMS} \sqrt{2} = 1.228 \sqrt{2} = 1.737 V_{pk} \quad (+1)$$

$$T = \frac{1}{f} = \frac{1}{1k} = 1 \text{ ms} \quad (+1)$$




$$I_{pk} = \frac{V_{pk}}{R} = \frac{1.737}{600} = 0.002895 \text{ or } 2.895 \text{ mA} \quad (+1)$$



$$P = \frac{V_{RMS}^2}{R} = \frac{1.228^2}{600} = 0.002513 \text{ or } 2.513 \text{ mW} \quad (+1)$$

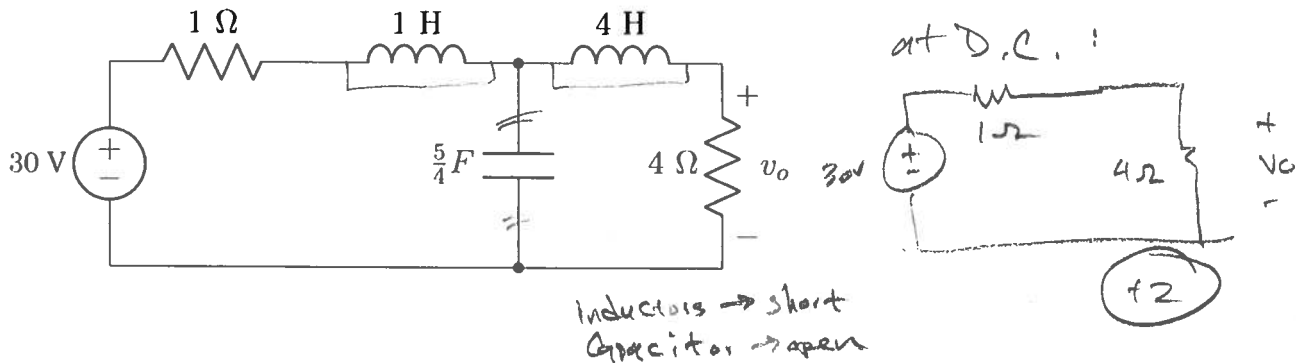5) Determine v_o , assuming the current source is operating at DC. Hint: redraw the circuit.



$$\therefore v_o = 30 \left(\frac{4}{1 + 4} \right) \quad (+2)$$

$$\therefore v_o = 24 \text{ V} \quad (+1)$$